

---

# **ECE380 Digital Logic**

## **Design of Finite State Machines Using CAD Tools**

## **FSM design using CAD tools**

---

- VHDL provides a number of constructs for designing finite state machines
- There is not a standard way for defining an FSM
- Basic approach
  - Create a user-defined data type to represent the possible states of an FSM
  - This signal represents the outputs (state variables) of the flip-flops that implement the states in the FSM
  - VHDL compiler chooses the appropriate number of flip-flops during the synthesis process
  - The state assignment can be done by the compiler or can be user specified

## User defined data types

---

- The **TYPE** keyword will be used to define a new data type used to represent states in the FSM

**TYPE State\_type IS (A, B, C);**

A user-defined  
data type definition

Data type  
name

Valid values for  
the data type

**Defines a data type (called State\_type) that can take on three distinct values: A, B, or C).**

## Representing states

---


- A **SIGNAL** is defined, of the user-defined **State\_type**, to represent the flip-flop outputs

**TYPE State\_type IS (A, B, C);  
SIGNAL y: State\_type;**

**The signal, y, can be used to represent the flip-flop outputs for an FSM that has three states**
 
## Design example

- Create a VHDL description for a circuit that detects a '11' input sequence on an input, **w**



**Recall the Moore state diagram for the circuit**

## VHDL design example

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY detect IS
    PORT(      clk, resetn, w : IN  STD_LOGIC ;
             z               : OUT STD_LOGIC) ;
END detect ;

ARCHITECTURE Behavior OF detect IS
    TYPE State_type IS (A,B,C) ;
    SIGNAL y: State_type ;
BEGIN

```

## VHDL design example continued

```
PROCESS ( resetn, clk )
BEGIN
  IF resetn = '0' THEN
    y <= A;
  ELSIF (clk'EVENT AND clk='1') THEN
    CASE y IS
      WHEN A =>
        IF w='0' THEN
          y <= A;
        ELSE
          y <= B;
        END IF;
      WHEN B =>
        IF w='0' THEN
          y <= A;
        ELSE
          y <= C;
        END IF;
    END CASE;
  END IF;
END PROCESS
z <= '1' WHEN y=C ELSE '0';
END Behavior;
```

## Alternative style of VHDL code

- Another form for describing the circuit in VHDL is to define two signals to represent the state of the FSM
  - One signal, **y\_present**, defines the present state of the FSM
  - The second, **y\_next**, defines the next state of the machine
- This notation follows the **y** (present state) and **Y** (next state) notation used previously
- Two PROCESS statements will be used to describe the machine
  - The first describes the STATE TABLE as a combinational circuit
  - The second describes the flip-flops, stating that **y\_present** should take on the value of **y\_next** after each positive clock edge

# Alternate VHDL description

```
ARCHITECTURE Behavior OF detect IS
    TYPE State_type IS (A,B,C);
    SIGNAL y_present, y_next: State_type;
BEGIN
    PROCESS(w,y_present)
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w='0' THEN
                    y_next <= A;
                ELSE
                    y_next <= B;
            WHEN B =>
                IF w='0' THEN
                    y_next <= A;
                ELSE
                    y_next <= C;
            WHEN C =>
                IF w='0' THEN
                    y_next <= A;
                ELSE
                    y_next <= C;
            END CASE;
        END PROCESS;
    PROCESS(clk,resetn)
    BEGIN
        IF resetn='0' THEN
            y_present <= A;
        ELSIF(clk'EVENT AND clk='1') THEN
            y_present <= y_next;
        END IF;
    END PROCESS
    z <= '1' WHEN y_present=C ELSE '0';
END Behavior;
```

# Specifying a state assignment

- With the previous designs, state assignment is done by the VHDL compiler
- State assignments can be user specified using the following constructs


```
ARCHITECTURE Behavior OF simple IS
    TYPE State_type IS (A, B, C) ;
    ATTRIBUTE ENUM_ENCODING : STRING ;
    ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11" ;
    SIGNAL y_present, y_next : State_type ;
BEGIN
```

Or

```
ARCHITECTURE Behavior OF simple IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
```
 
## VHDL code of a Mealy FSM

- A Mealy FSM can be described in a similar manner as a Moore FSM
- The state transitions are described in the same way as the original VHDL example
- The major difference in the case of a Mealy FSM is the way in which the code for the output is written
- Recall the Mealy state diagram for the '11' sequence detector



## Mealy '11' detector VHDL code

```

ARCHITECTURE Behavior OF detect IS
    TYPE State_type IS (A,B) ;
    SIGNAL y: State_type ;
BEGIN
    PROCESS(resetn,clk)
    BEGIN
        IF resetn='0' THEN
            y <= A;
        ELSEIF(clk'EVENT AND clk='1') THEN
            CASE y IS
                WHEN A =>
                    IF w='0' THEN y<= A;
                    ELSE y<= B;
                    END IF;
                WHEN B =>
                    IF w='0' THEN y<= A;
                    ELSE y<= B;
                    END IF;
            END CASE;
        END IF;
    END PROCESS;
    PROCESS(y,w)
    BEGIN
        CASE y IS
            WHEN A =>
                z <='0';
            WHEN B =>
                z <= w;
            END CASE;
        END PROCESS;
    END Behavior;

```