

---

# ECE380 Digital Logic

## Flip-Flops, Registers and Counters: Flip-Flops


## Flip-flops

---

- The gated latch circuits presented are level sensitive and can change states more than once during the 'active' period of the clock signal
- Circuits (storage elements) that can change their state no more than once during a clock period are also useful
- Two types of circuits with such behavior
  - Master-slave flip-flop
  - Edge-triggered flip-flop
 
## Master-slave D flip-flop



- Consists of 2 gated D latches
  - The first, **master**, changes its state while clock=1
  - The second, **slave**, changes its state while clock=0



## Master-slave D flip-flop



- When clock=1, the master tracks the values of the D input signal and the slave does not change
  - Thus  $Q_m$  follows any changes in D and  $Q_s$  remains constant
- When the clock signal changes to 0, the master stage stops following the changes in the D input signal
- At the same time, the slave stage responds to the value of  $Q_m$  and changes states accordingly
- Since  $Q_m$  does not change when clock=0, the slave stage undergoes at most one change of state during a clock cycle
- From an output point of view, the circuit changes  $Q_s$  (its output) at the **negative edge** of the clock signal

# Master-slave D flip-flop

  
  
# Edge-triggered flip-flop

- A circuit, similar in functionality to the master-slave D flip-flop, can be constructed with 6 NAND gates





Positive-edge-triggered  
D type flip-flop


24 transistors
  
## Edge-triggered flip-flop

- The previous circuit responds on the positive edge of the clock signal
- A negative-edge triggered D flip-flop can be constructed by replacing the NAND with NOR gates




## Comparing D storage elements

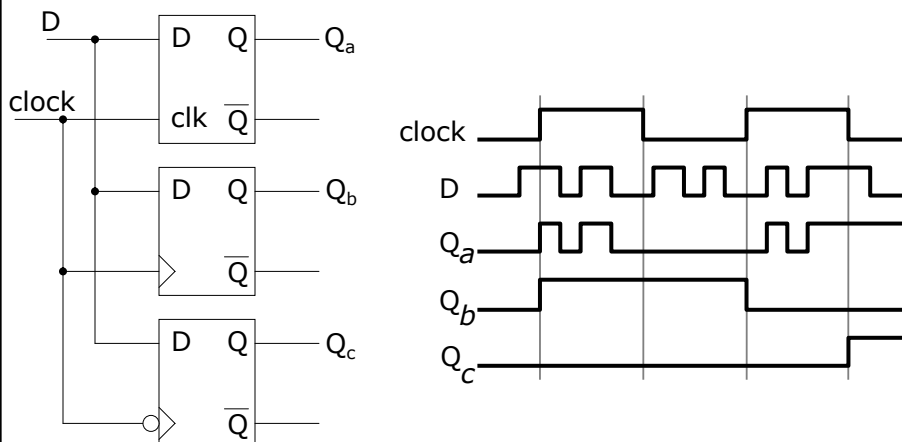
 
## Clear and preset inputs

- It may be desirable to specifically set ( $Q=1$ ) or clear ( $Q=0$ ) a flip-flop
- Practical flip-flops often have **preset** and **clear** inputs
  - Generally, these inputs are **asynchronous** (they do not depend on the clock signal)




As long as  $\text{Preset}'=0$ ,  $Q=1$

As long as  $\text{Clear}'=0$ ,  $Q=0$

 
## T flip-flop

- Another flip-flop type, the **T flip-flop**, can be derived from the basic D flip-flop presented
- Feedback connections make the input signal D equal to the value of Q or Q' under control of a signal labeled T


 
## T flip-flop


- The name T derives from the behavior of the circuit, which 'toggles' its state when  $T=1$ 
  - This feature makes the T flip-flop a useful element when constructing counter circuits




## JK flip-flop

- The **JK flip-flop** can also be derived from the basic D flip-flop such that
$$D = JQ' + K'Q$$
- The JK flip-flop combines aspects of the SR and the T flip-flop
  - It behaves as the SR flip-flop (where  $J=S$  and  $K=R$ ) for all values except  $J=K=1$
  - For  $J=K=1$ , it toggles like the T flip-flop

# JK flip-flop

 

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

 

Positive edge triggered

# JK flip-flop timing diagram

Complete the following timing diagram

