

---

# ECE380 Digital Logic

Implementation Technology:  
Buffers, Tri-state gates,  
Transmission gates


## Buffers

---

- In circuits where a logic gate has to drive a large capacitive load, **buffers** are often used to improved performance
- Buffers can be created with different amounts of drive capability (depending on the size of the transistors used to construct them)
  - Larger transistors => more current handling capability
  - A common use of a buffer is to control a light-emitting diode (LED)
- Buffers have greater **fan-out** than other (regular) logic gates


# Buffers

---

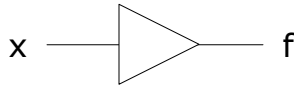

$$f=x$$

A non-inverting buffer

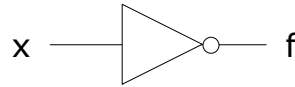


$$f=x'$$

An inverting buffer
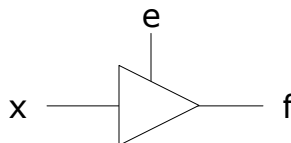
## Tri-state Buffers (Gates)

---

- A tri-state buffer (gate) has
  - One input (x)
  - One output (f)
  - One control input (e)




$$f=x \text{ if } e=1$$

A tri-state buffer
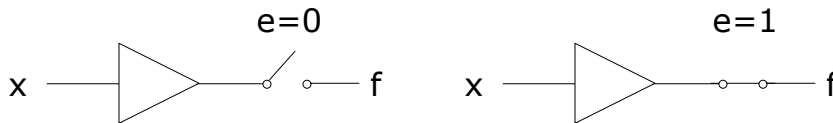
## Tri-state Buffers (Gates)

- When  $e=1$ , the buffer drives the value of  $x$  onto  $f$ , causing  $f=x$
- When  $e=0$ , the buffer is completely disconnected from the output  $f$



Equivalent circuit

## Tri-state Buffers (Gates)





- In truth table form,
- For the rows where  $e=0$ , the output is denoted by the logic value  $Z$
- This  $Z$  is called the high-impedance state
- The name tri-state derives from the fact that there are two normal states for a logic signal (0 and 1) and  $Z$  represents a third state that has no output

$e$	$x$	$f$
0	0	$Z$
0	1	$Z$
1	0	0
1	1	1


## Four type of tri-state buffers

- There are four possible configurations of tri-state buffers
  - based on two types of outputs
    - Inverting and non-inverting outputs
  - and two types of control signals (e)
    - Active high and active low enables
- Active low enables implies the output is active ( $f=x$ ) when the enable is low ( $e=0$ )

## Four type of tri-state buffers

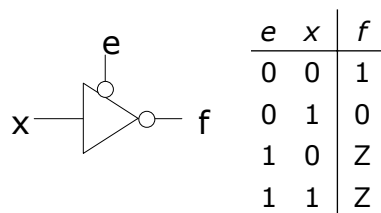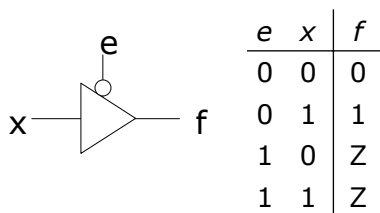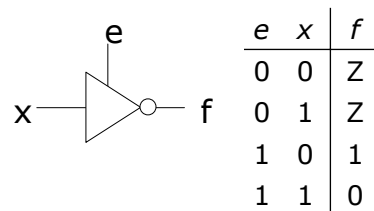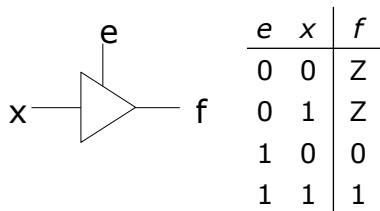

# Tri-state buffer application



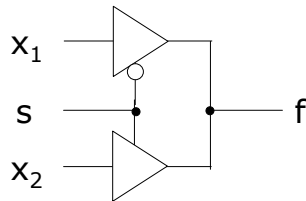


s	x1	x2	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Note the outputs of the tri-state gates are wired together
  - This is possible only because we know that (in this configuration) one or the other of the tri-state gates will be in the high impedance (Z) state
  - This type of wired connection is not possible with ordinary logic gates

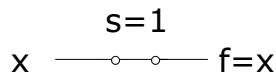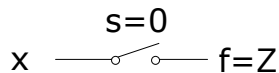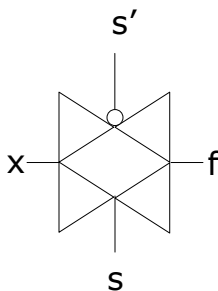
# Transmission gate

- A **transmission gate** acts as a switch, connecting an input (x) to an output (f)
  - Commonly used to implement XOR gate and multiplexer circuits



s	f
0	Z
1	x

## Multiplexer with transmission gates

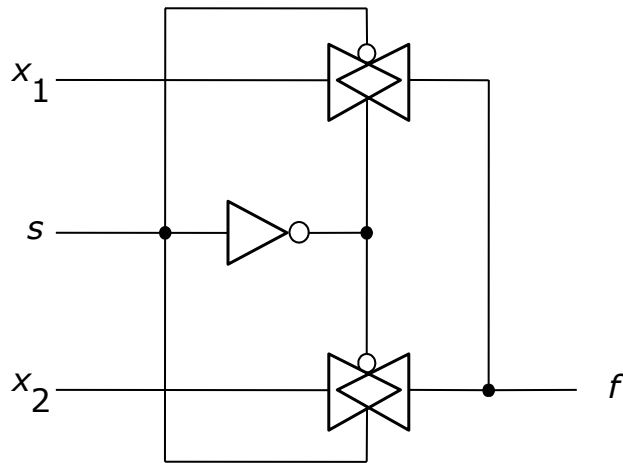

## XOR with transmission gates

