
ECE380 Digital Logic

Flip-Flops, Registers and
Counters:
Latches

Storage elements


- Previously, we have considered ***combinational circuits*** where the output values depend only on the values of signals applied to the inputs
- Another class of logic circuits have the property that the outputs depend not only on the current inputs, but also on the past behavior of the circuit
- Such circuits include ***storage elements*** that store the values of logic signals

Sequential circuits


- Contents of the storage elements represent the **state** of the circuit
- Input value changes may leave the circuit in the same state or cause it to change to a new state
- Over time, the circuit changes through a sequence of states as a result of changes in the inputs
- Circuits that exhibit this behavior are referred to as **sequential circuits**

Alarm control system

 
- Suppose we wish to construct an alarm circuit such that the output remains active (on) even after the sensor output that triggered the alarm goes off
 - A typical car alarm is representative of this type of circuit
- The circuit requires a memory element to remember that the alarm has to be active until a **reset** signal arrives



A simple memory element

 


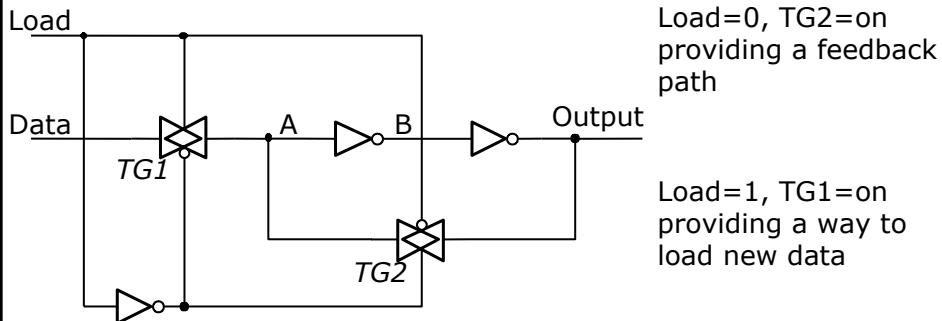Simple memory element: feedback path provides basis for the 'remembering' of data




Basic SR latch

 - A similar circuit, constructed with NOR gates can also be constructed
- Inputs, **Set** and **Reset**, provide the means to changing the state, **Q**, of the circuit
- This circuit is referred to as a basic **latch**




Basic SR latch

 - When $R=S=0$ the circuit remains in its current state (either $Q_a=1$ and $Q_b=0$ or $Q_a=0$ and $Q_b=1$)
- When $S=1$ and $R=0$, the latch is **set** into a state where $Q_a=1$ and $Q_b=0$
- When $S=0$ and $R=1$, the latch is **reset** into a state where $Q_a=0$ and $Q_b=1$
- Where $S=1$ and $R=1$, $Q_a=Q_b=0$ (there are actually problems with this state as we will see)



S	R	Q_a	Q_b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

Basic SR latch timing diagram

 


Basic SR latch timing diagram

- If the **propagation delays** from Q_a and Q_b are exactly the same, the oscillation at time t_{10} would continue indefinitely
- In a real circuit there would probably be some (mostly insignificant) difference in the delays and the latch would eventually settle into one of its two stable states (but we don't know which one it would be)
- Thus the $S=R=1$ combination is generally considered an **unallowed** combination in the SR latch

Gated SR latch


- The basic SR latch changes its state whenever its inputs change
- It may be desirable to add an enable signal to the basic SR latch that allows us to control when the circuit can change states
- Such a circuit is referred to as a ***gated SR latch***

Gated SR latch circuit

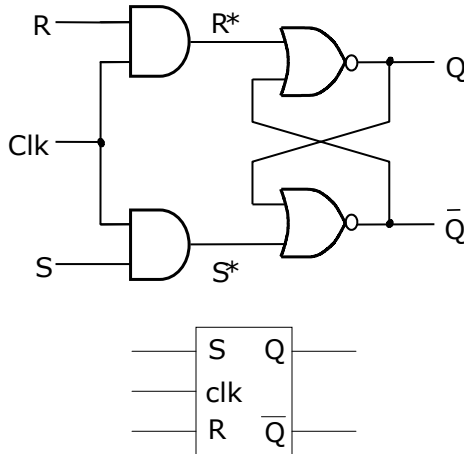


CLK	S	R	Q(t+1)
0	X	X	Q(t)
1	0	0	Q(t)
1	0	1	0
1	1	0	1
1	1	1	X


Q(t)=present state
Q(t+1)=next state

 

Gated SR latch timing diagram

 


Gated SR latch with NAND gates

 


Gated D latch

 
- Another useful latch has a single data input, **D**, and it stores the value of this input under the control of a clock signal
- This is referred to as a ***gated D latch***
 - Useful in circuits where we want to store some value
 - The output of an adder/subtractor circuit would be one example



Gated D latch

 

CLK	D	Q(t+1)
0	X	Q(t)
1	0	0
1	1	1

 

Level versus edge sensitivity

- Since the output of the D latch is controlled by the level (0 or 1) of the clock input, the latch is said to be **level sensitive**
 - All of the latches we have seen have been level sensitive
- It is possible to design a storage element for which the output only changes at the point in time when the clock changes from one value to another
- Such circuits are said to be **edge triggered**

Effects of propagation delays

- Previously we have ignored the effects of propagation delay. In practical circuits, it is essential to account for these delays
- For the gated D latch (and others as well), it is important that the value of D not change at the time the clock (clk) goes from 1 to 0
 - The designer must make sure the signal is stable when the critical change in the clock takes place
- The minimum time the D signal must remain stable prior to the negative edge (1→0) of the clock signal is called the **setup time** (t_{su})
- The minimum time the D signal must remain stable after the negative edge of clock is the **hold time** (t_h)
 - Typical CMOS values are: $t_{su}=3\text{ns}$ and $t_h=2\text{ns}$

Setup and hold times

