

---

# **ECE380 Digital Logic**

Combinatorial Circuit Building  
Blocks:  
VHDL for Combinational Circuits

## **Assignment statements**

---

- VHDL provides several types of statements that can be used to assign logic values to signals
  - Simple assignment statements
    - Used previously, for logic or arithmetic expressions
  - Selected signal assignments
  - Conditional signal assignments
  - Generate statements
  - If-then-else statements
  - Case statements

## Selected signal assignment

---

- A selected signal assignment allows a signal to be assigned one of several values, based on a selection criterion
  - Keyword **WITH** specifies that **s** is used for the selection criterion
  - Two **WHEN** clauses state that  $f=w_0$  when  $s=0$  and  $f=w_1$  otherwise
  - The keyword **OTHERS** must be used

```
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <=    w0 WHEN '0',
               w1 WHEN OTHERS;
END Behavior;
```

## 4-to-1 multiplexer VHDL code

---

```
ENTITY mux4to1 IS
    PORT ( w      : IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
          s      : IN  STD_LOGIC_VECTOR(1 DOWNTO 0);
          f      : OUT STD_LOGIC );
END mux4to1;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <=    w(0) WHEN "00",
               w(1) WHEN "01",
               w(2) WHEN "10",
               w(3) WHEN OTHERS;
END Behavior;
```

## 2-to-4 binary decoder VHDL code

```
ENTITY dec2to4 IS
  PORT ( w      : IN   STD_LOGIC_VECTOR(1 DOWNTO 0);
        En      : IN   STD_LOGIC;
        y      : OUT  STD_LOGIC_VECTOR(0 TO 3));
END dec2to4;
ARCHITECTURE Behavior OF dec2to4 IS
  SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0);
BEGIN
  Enw <= En & w;
  WITH Enw SELECT
    y <=  "1000" WHEN "100",
          "0100" WHEN "101",
          "0010" WHEN "110",
          "0001" WHEN "111",
          "0000" WHEN OTHERS;
END Behavior;
```

## Conditional signal assignment

- Similar to the selected signal assignment, a ***conditional signal assignment*** allows a signal to be set to one of several values
  - Uses **WHEN** and **ELSE** keyword to define the condition and actions

```
ENTITY mux2to1 IS
  PORT (w0, w1, s : IN   STD_LOGIC;
        f         : OUT  STD_LOGIC );
END mux2to1;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
  f <= w0 WHEN s = '0' ELSE w1;
END Behavior;
```

## Priority encoder VHDL code

---

```
ENTITY priority IS
  PORT (    w      : IN   STD_LOGIC_VECTOR(3 DOWNTO 0);
          y      : OUT  STD_LOGIC_VECTOR(1 DOWNTO 0);
          z      : OUT  STD_LOGIC );
END priority;

ARCHITECTURE Behavior OF priority IS
BEGIN
  y <="11" WHEN w(3) = '1' ELSE
    "10" WHEN w(2) = '1' ELSE
    "01" WHEN w(1) = '1' ELSE
    "00";
  z <='0' WHEN w = "0000" ELSE '1';
END Behavior;
```

## Generate statements

---

- Whenever we write structural VHDL code, we often create ***instances*** of a particular ***component***
  - The ripple carry adder was one example
- If we need to create a large number of instances of a component, a more compact form is desired
- VHDL provides a feature called the **FOR GENERATE** statement
  - This statement provides a loop structure for describing regularly structured hierarchical code

## 4-bit ripple carry adder

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;
ENTITY adder4 IS
    PORT ( Cin      : IN    STD_LOGIC ;
           X, Y      : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           S         : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           Cout      : OUT   STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin,  X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

## 4-bit ripple carry adder

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;
ENTITY adder4 IS
    PORT ( Cin      : IN    STD_LOGIC ;
           X, Y      : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           S         : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           Cout      : OUT   STD_LOGIC ) ;
END adder4 ;
ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(0 TO 4) ;
BEGIN
    C(0) <= Cin ;
    Cout <= C(4) ;
    G1: FOR i IN 0 TO 3 GENERATE
        stages: fulladd PORT MAP (
            C(i), X(i), Y(i), S(i), C(i+1)) ;
    END GENERATE ;
END Structure ;
```

## Process statement

---

- We have introduced several types of assignment statements
  - All have the property that the order in which they appear in VHDL code does not affect the meaning of the code
- Because of this property, these statements are called ***concurrent assignment statements***
- VHDL provides a second category of statements, ***sequential assignment statements***, for which the ordering of the statements may affect the meaning of the code
  - **If-then-else** and **case** statements are sequential
- VHDL requires that sequential assignment statements be placed inside another statement, the ***process*** statement

## Process statement

---

- The process statement, or simply process, begins with the **PROCESS** keyword, followed by a parenthesized list of signals called the ***sensitivity list***
  - This list includes all the signals used inside the process
- Statements inside the process are evaluated in sequential order
- Assignments made inside the process are not visible outside the process until all statements in the process have been evaluated
  - If there are multiple assignments to the same signal inside a process, only the last one has any visible effect

## 2-to-1 MUX as a PROCESS

ARCHITECTURE Behavior OF mux2to1 IS

BEGIN

**PROCESS** ( w0, w1, s )

**BEGIN**

IF s = '0' THEN

f <= w0 ;

ELSE

f <= w1 ;

END IF ;

**END PROCESS** ;

END Behavior ;

**Sensitivity list,  
Whenever a list entry  
changes, the process  
is reevaluated  
(activated)**

IF-THEN-ELSE statement  
to implement the MUX  
function

## Priority encoder (IF-THEN-ELSE)

ARCHITECTURE Behavior OF priority IS

BEGIN

**PROCESS** ( w )

**BEGIN**

IF w(3) = '1' THEN

y <= "11" ;

ELSIF w(2) = '1' THEN

y <= "10" ;

ELSIF w(1) = '1' THEN

y <= "01" ;

ELSE

y <= "00" ;

END IF ;

**END PROCESS** ;

z <= '0' WHEN w = "0000" ELSE '1' ;

END Behavior ;

# Priority encoder (alternative)

```


ARCHITECTURE Behavior OF priority IS
BEGIN
  PROCESS ( w )
  BEGIN
    y <= "00" ;
    IF w(1) = '1' THEN y <= "01" ; END IF ;
    IF w(2) = '1' THEN y <= "10" ; END IF ;
    IF w(3) = '1' THEN y <= "11" ; END IF ;

    z <= '1' ;
    IF w = "0000" THEN z <= '0' ; END IF ;
  END PROCESS ;
END Behavior ;
  
```
 
# Implied memory in a PROCESS


```

ARCHITECTURE Behavior OF c1 IS
BEGIN
  PROCESS ( A, B )
  BEGIN
    AeqB <= '0' ;
    IF A = B THEN
      AeqB <= '1' ;
    END IF ;
  END PROCESS ;
END Behavior ;
  
```



```

 ARCHITECTURE Behavior OF c1 IS
BEGIN
  PROCESS ( A, B )
  BEGIN
    IF A = B THEN
      AeqB <= '1' ;
    END IF ;
  END PROCESS ;
END Behavior ;
  
```





## Case statement

---

- A **case statement** is similar to a selected assignment statement in that the case statement has a selection signal and includes WHEN clauses for various valuations of the selection signal
  - Begins with a **CASE** keyword
  - Each **WHEN** clause specifies the statements that should be evaluated when the selection signal has a specified value
  - The case statement must include a when clause for all valuations of the selection signal
    - Use the **OTHERS** keyword

## 2-to-1 MUX with CASE

---

**ARCHITECTURE Behavior OF mux2to1 IS**

**BEGIN**

**PROCESS ( w0, w1, s )**

**BEGIN**

**CASE s IS**

**WHEN '0' =>**

**f <= w0 ;**

**WHEN OTHERS =>**

**f <= w1 ;**

**END CASE ;**

**END PROCESS ;**

**END Behavior ;**

## 2-to-4 binary decoder with CASE

---

**ARCHITECTURE Behavior OF dec2to4 IS**

**BEGIN**

**PROCESS ( w, En )**

**BEGIN**

**IF En = '1' THEN**

**CASE w IS**

**WHEN "00" => y <= "1000" ;**

**WHEN "01" => y <= "0100" ;**

**WHEN "10" => y <= "0010" ;**

**WHEN OTHERS => y <= "0001" ;**

**END CASE ;**

**ELSE**

**y <= "0000" ;**

**END IF ;**

**END PROCESS ;**

**END Behavior ;**