

---

# ECE380 Digital Logic

## Flip-Flops, Registers and Counters: Registers and Counters


## Registers

---

- A flip-flop stores one bit of information
- When a set of  $n$  flip-flops is used to store  $n$  bits of data, we refer to these flip-flops as a **register**
  - Common register usages include
    - Holding a data value output from an arithmetic circuit
    - Holding a count value in a counter circuit
- A common clock signal is typically used for each flip-flop in a register
 
# Shift register

- A register that provides the ability to shift its contents by a single bit
  - May be to the right or left (or possibly both)



Shift right register

# Shift right register


- Data is shifted to the right in a serial fashion using the **In** input
- Positive edge triggered
  - Contents of each flip-flop are transferred to the next flip-flop at each positive edge of the clock
- Level sensitive devices would not be appropriate for this circuit

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>
t <sub>0</sub>	1	0	0	0	0
t <sub>1</sub>	0	1	0	0	0
t <sub>2</sub>	1	0	1	0	0
t <sub>3</sub>	1	1	0	1	0
t <sub>4</sub>	1	1	1	0	1
t <sub>5</sub>	0	1	1	1	0
t <sub>6</sub>	0	0	1	1	1
t <sub>7</sub>	0	0	0	1	1

## Parallel-access shift register

- Data transfer in computer systems is a common function
  - If the transfer is  $n$ -bits at a time, the transfer is said to be in **parallel**
  - If the transfer is 1-bit at a time, the transfer is said to be **serial**
- To transfer data serially, data is loaded into a register in parallel (in one clock cycle) and then shifted out one bit at a time
  - Parallel-to-serial data conversion
- If bits are received serially, after  $n$  clock cycles the contents of a register can be accessed in parallel as an  $n$ -bit item
  - Serial-to-parallel conversion


## Parallel-access shift register

 


# Counters

- Special purpose arithmetic circuits used for the purpose of counting
  - Design circuits that can increment or decrement a count by 1
- Counter circuits server many purposes
  - Count occurrences of certain events
  - Generate timing intervals for controlling various tasks in a digital system
  - Track elapsed time between events
- Often (but not always) built with T flip-flops because the toggle feature is naturally suited for implementing the counting operation

## Up-counter with T flip-flops

 

## Down counter with T flip-flops

 

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 26-9

## Asynchronous counters

- The previous counters are examples of **asynchronous** counters. Also called **ripple** counters.
  - Input clock is only connected to one flip-flop
  - Clocks for other flip-flops are (or are derived from) the outputs of the previous flip-flops
- This form of counter is slow because the cascaded clocking scheme
  - The clock source ripples from stage-to-stage
  - The ripple effect is similar to that of a ripple carry adder circuit

Electrical & Computer Engineering


Dr. D. J. Jackson Lecture 26-10

# Synchronous counters

- Synchronous counters are built by clocking all the flip-flops at the same time (with a single clocking source)
  - Faster response than asynchronous counters
- Synchronous counters with T flip-flops
  - Least significant bit,  $Q_0$ , changes every clock cycle
  - Bit one,  $Q_1$ , only changes when  $Q_0=1$
  - Bit two,  $Q_2$ , only changes when  $Q_0=Q_1=1$

	$Q_2$	$Q_1$	$Q_0$	
0	0	0	0	
1	0	0	1	$Q_1$ changes
2	0	1	0	
3	0	1	1	
4	1	0	0	$Q_2$ changes
5	1	0	1	
6	1	1	0	
7	1	1	1	
8	0	0	0	


# T flip-flop synchronous counter

 

4-bit synchronous up counter
 
## Enable and clear capability


- It may be desirable to disable counting or clear the counter
  - Include an **enable** control signal
  - Use a flip-flop with asynchronous clear capability



## D flip-flop synchronous counter

- A 4-bit up counter counts in the sequence 0,1,2,...,15,0,1...
- The count is given by the flip-flop outputs  $Q_3Q_2Q_1Q_0$
- The D inputs are given by:
  - $D_0 = Q_0 \oplus \text{Enable}$
  - $D_1 = Q_1 \oplus Q_0 \cdot \text{Enable}$
  - $D_2 = Q_2 \oplus Q_1 \cdot Q_0 \cdot \text{Enable}$
  - $D_3 = Q_3 \oplus Q_2 \cdot Q_1 \cdot Q_0 \cdot \text{Enable}$

## Four-bit counter (D flip-flops)

 

## Counters with parallel load

- It is common for counters to begin a count with a zero value
  - An asynchronous **clear** input can be used for this purpose
- It may be desirable for a counter to begin with a non-zero value
- Adding circuitry to provide **parallel load** capability is necessary
- A control input, **load**, is used to select a mode of operation
  - Load=0, circuit counts
  - Load=1, parallel load a new value into the counter



# Parallel load counter

