 

ECE380 Digital Logic

Combinatorial Circuit Building Blocks: Multiplexers


Multiplexers

- A multiplexer (MUX) circuit has
 - A number of data inputs
 - One (or more) select inputs
 - One output
- It passes the signal value on one of its data inputs to its output based on the value(s) of the select signal(s)




s	$f(s, x_1, x_2)$
0	x_1
1	x_2

Multiplexer implementations

 

4-input multiplexer

 - A 4-input multiplexer 'selects' one of four data inputs to be output based on the values of 2 select lines




s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

$$f = s_1' s_0' w_0 + s_1' s_0 w_1 + s_1 s_0' w_2 + s_1 s_0 w_3$$


Building a 4-input MUX

 - A 4-input multiplexer can be constructed using 2-input multiplexers




MUX application (a 2x2 crossbar)

- A circuit with n inputs and k outputs whose function is to provide a capability to connect any input to any output is called a **$n \times k$ crossbar switch**
 - With 2 inputs and 2 outputs, it is called a 2x2 crossbar
 - Useful in applications where it is necessary to connect one set of wires to another set of wires, where the connection pattern changes from time to time
 - Telephone switching networks are an example

 


MUX application (prog. switch)

 - In programmable devices (PLDs, CPLDs and FPGAs) programmable switches connect wires inside the device
 - These can be implemented with multiplexers



 An FPGA logic block with programmable inputs




MUX implementation

Logic functions using MUXs


- MUXs can be used to synthesize logic functions
 - The LUT implementations use MUXs to select a (constant) value from a look-up table
- Consider the XOR function

<i>a</i>	<i>b</i>	<i>f</i>
0	0	0
0	1	1
1	0	1
1	1	0

 

Logic functions using MUXs

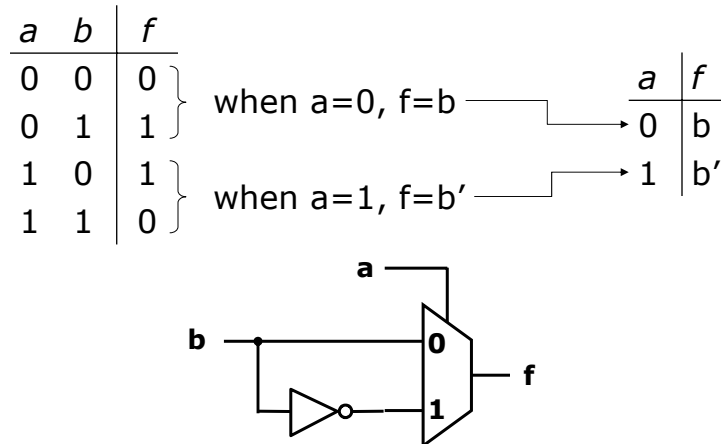- The previous XOR solution is not particularly efficient




Logic functions using MUXs

- Implement the following with a 2-input MUX and any additional logic gates

a	b	f
0	0	1
0	1	1
1	0	0
1	1	1

Logic functions using MUXs

 - A 3-input XOR can be implemented with two 2-input MUXs



Logic functions using MUXs

- Implement the following with 2-input MUXs and any additional logic gates

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Shannon's expansion theorem

- Any Boolean function $f(w_1, \dots, w_n)$ can be written in the form

$$f(w_1, \dots, w_n) = (w_1)' \cdot f(0, w_2, \dots, w_n) + (w_1) \cdot f(1, w_2, \dots, w_n)$$
- The expansion can be done using any of the n variables

- If $f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$
 – Expanding this in terms of w_1 gives

$$f(w_1, w_2, w_3) = \underbrace{w_1(w_2 + w_3)}_{f \text{ when } w_1=1} + \underbrace{(w_1)'(w_2 w_3)}_{f \text{ when } w_1=0}$$


f when $w_1=1$

f when $w_1=0$

Shannon's expansion example

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

 

Shannon's expansion example


x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$f = x'y'z' + x'y'z + x'yz + xy'z' + xy'z$$

choose x as the expansion variable

$$f = x'(y'z' + y'z + yz) + x(y'z' + y'z)$$

$$f = x'(y' + z) + x(y')$$

 

Shannon's expansion example

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$f = x'y'z' + x'y'z + x'yz + xy'z' + xy'z$$

choose z as the expansion variable