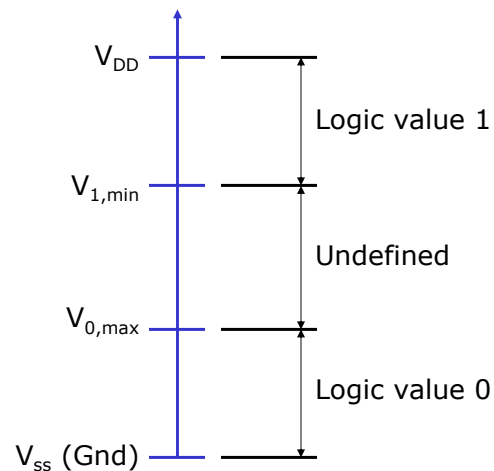

ECE380 Digital Logic

Implementation Technology:
NMOS and PMOS Transistors,
CMOS logic gates

Logic values as voltage levels

- V_{ss} is the minimum voltage that can exist in the system. We will use $V_{ss}=0V$.
- V_{DD} is the power supply voltage. We will use $V_{DD}=+5V$. $V_{DD}=+3.3V$ is also common.
- Exact levels of $V_{0,max}$ and $V_{1,min}$ depend on the implementation technology





Transistor switches

- Logic circuits are built with transistors
- We will assume a transistor operates as a simple switch controlled by a logic signal x
- The most popular type of transistor for implementing a simple switch is the **metal oxide semiconductor field effect transistor** (MOSFET)
- Two types of MOSFETs
 - N-channel (**NMOS**)
 - P-channel (**PMOS**)
- Early circuits relied on NMOS or PMOS transistors, but not both
- Current circuits use both NMOS and PMOS transistors in a configuration called **complementary MOS** (CMOS)



NMOS transistor as a switch



  A simple switch controlled by the input x



NMOS transistor as a switch

 
 


- The transistor operates by controlling the voltage V_G at the gate terminal
- If V_G is low, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If V_G is high, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.



PMOS transistor as a switch



  A simple switch controlled by the input x




PMOS transistor as a switch

  

- The transistor operates by controlling the voltage V_G at the gate terminal
- If V_G is high, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If V_G is low, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.

NMOS and PMOS in logic circuits

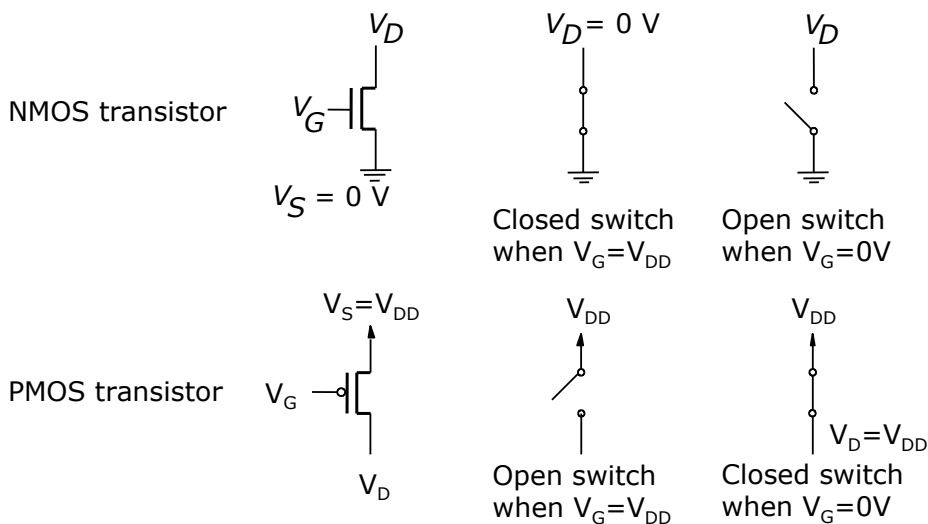

NMOS and PMOS in logic circuits


- When the NMOS transistor is turned on, its drain is ***pulled down to Gnd***
- When the PMOS transistor is turned on, its drain is ***pulled up to V_{DD}***
- Because of the way transistors operate:
 - An NMOS transistor cannot be used to pull its drain terminal completely up to V_{DD}
 - A PMOS transistor cannot be used to pull its drain terminal completely down to Gnd
- Therefore, NMOS and PMOS transistors are commonly used in pairs in CMOS circuits

CMOS logic gates


- A CMOS logic gate involves NMOS transistors in a ***pull-down network*** (PDN) and PMOS transistors in a ***pull-up network*** (PUN)
- The functions realized by the PDN and PUN networks are complements of one another
- The PDN and PUN have equal numbers of transistors, which are arranged so that the two networks are duals of one another
 - Wherever the PDN has NMOS transistors in series, the PUN has PMOS transistors in parallel, and vice versa

CMOS logic gates

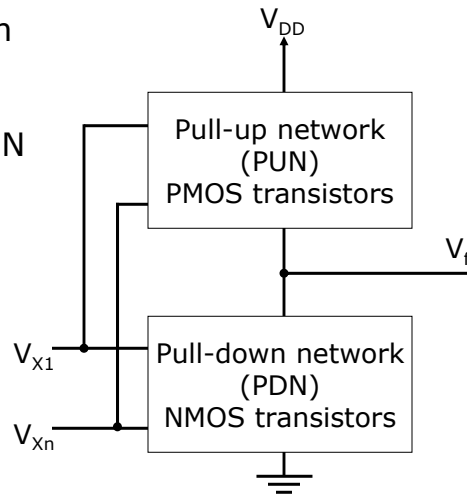
- For any given valuation of the input signals, either the PDN pulls V_f down to Gnd or the PUN pulls V_f up to V_{DD}



CMOS NOT gate

 


x	T1	T2	f
0	On	Off	1
1	Off	On	0

 

2 transistors


CMOS NAND gate

 

X1	X2	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	1
1	0	Off	On	On	Off	1
1	1	Off	Off	On	On	0

4 transistors


CMOS NOR gate

 

X1	X2	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	0
1	0	Off	On	On	Off	0
1	1	Off	Off	On	On	0


4 transistors

CMOS AND gate

 


6 transistors

CMOS OR gate

 


6 transistors

CMOS non-inverting buffer


 


A non-inverting buffer

 

4 transistors


CMOS transmission gate

  


s	f
0	Z
1	x

2 transistors

CMOS tri-state buffer

 

<i>e</i>	<i>x</i>	<i>f</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

 

8 transistors